

## Homework 3

### Problem 3.1

**Solution:**

Distributive Law: DL

Identity Law: IL

Annulment Law: AL

Complement Law: CL

De Morgan's Theorem: DM

Double Negation Law: DN

**a)**

$$x = (M + N)(\overline{M} + P)(\overline{N} + \overline{P}) =$$

$$DL := (M\overline{M} + MP + N\overline{M} + NP)(\overline{N} + \overline{P}) =$$

$$IL := (MP + N\overline{M} + NP)(\overline{N} + \overline{P}) =$$

$$DL := MP\overline{N} + MP\overline{P} + N\overline{M}\overline{N} + N\overline{M}\overline{P} + NP\overline{N} + NP\overline{P}$$

$$IL := M\overline{N}P + \overline{M}N\overline{P}$$

**b)**

$$z = \overline{A}B\overline{C} + AB\overline{C} + B\overline{C}D =$$

$$DL := B\overline{C}(\overline{A} + A + D) =$$

$$CL := B\overline{C}(1 + D) =$$

$$AL := B\overline{C}$$

**c)**

$$x = \overline{(M + N + P)Q} =$$

$$DM := \overline{M + N + P} + \overline{Q} =$$

$$DM := \overline{M} * \overline{N} * \overline{P} + \overline{Q}$$

**d)**

$$z = \overline{ABC + DEF} =$$

$$DM := \overline{ABC} * \overline{DEF} =$$

$$DM := (\overline{A} + \overline{B} + \overline{C}) * (\overline{D} + \overline{E} + \overline{F})$$

**e)**

$$z = \overline{AB + CD + EF} =$$

$$DM := \overline{AB} * \overline{CD} * \overline{EF} =$$

$$DM := (\overline{A} + \overline{B}) * (\overline{C} + \overline{D}) * (\overline{E} + \overline{F}) =$$

$$DN := (\overline{A} + B) * (\overline{C} + D) * (\overline{E} + F)$$

f)

Throughout this problem, we use De Morgan's Theorem in every step and DN in some of the steps where we have double negation:

$$\begin{aligned}
 z &= \overline{\overline{A + B\overline{C}} + D(E + \overline{F})} = \\
 &= \overline{\overline{A + B\overline{C}}} * \overline{D * (E + \overline{F})} = \\
 &= \overline{A * B * \overline{C}} * \overline{D * E * \overline{F}} = \\
 &= \overline{A} * (\overline{B + \overline{C}}) * \overline{D\overline{E}F} = \\
 &= \overline{A} * (\overline{B + C}) * (\overline{D\overline{E}F}) = \\
 &= (\overline{A} + \overline{B + C}) * (\overline{D} + \overline{\overline{E}} + \overline{F}) = \\
 &= (A + \overline{B} * \overline{C}) * (\overline{D} + E + \overline{F}) = \\
 &= (A + B * \overline{C}) * (\overline{D} + E + \overline{F})
 \end{aligned}$$

### Problem 3.2

**Solution:**

Firstly, we obtain the following boolean expression from analyzing the circuit:

$$x = (\overline{A} \wedge \overline{B} \wedge D) \vee (A \wedge \overline{B} \wedge \overline{C}) \vee (\overline{A} \wedge \overline{B} \wedge \overline{C})$$

Now, from the expression above, we can create the Karnaugh Map by using gray encoding and plotting the 1s correspondingly.


Karnaugh map

	$\overline{cd}$	$\overline{cd}$	$cd$	$c\overline{d}$
$\overline{a}b$	1	1	1	0
$\overline{a}b$	0	0	0	0
$\overline{a}b$	0	0	0	0
$\overline{a}b$	1	1	0	0

After grouping the 1s in three different groups (two groups with two 1s and a group with a single 1) and analyzing the Karnaugh Map, we get the following simplified boolean expression:  
 $\overline{A}BD + \overline{B}C$

### Problem 3.3


Solution:

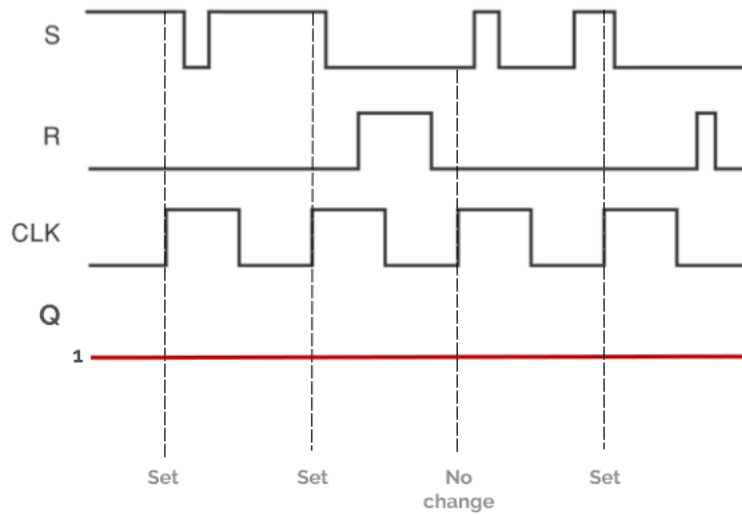

Inputs			Output
S	R	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous

### Problem 3.4


Solution:

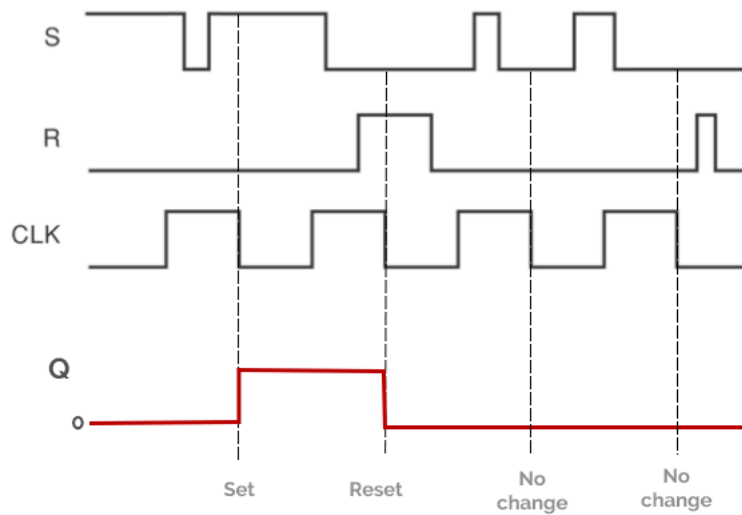

Inputs			Output
S	R	CLK	Q
0	0	↓	$Q_0$ (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	Ambiguous

Problem 3.5


Solution:

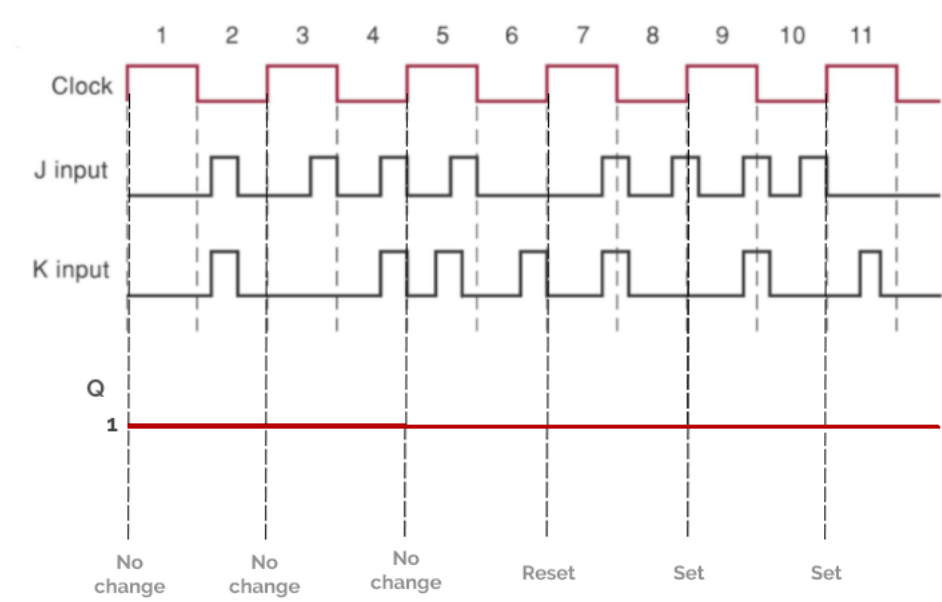

J	K	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\overline{Q_0}$ (toggles)

Problem 3.6


Solution:

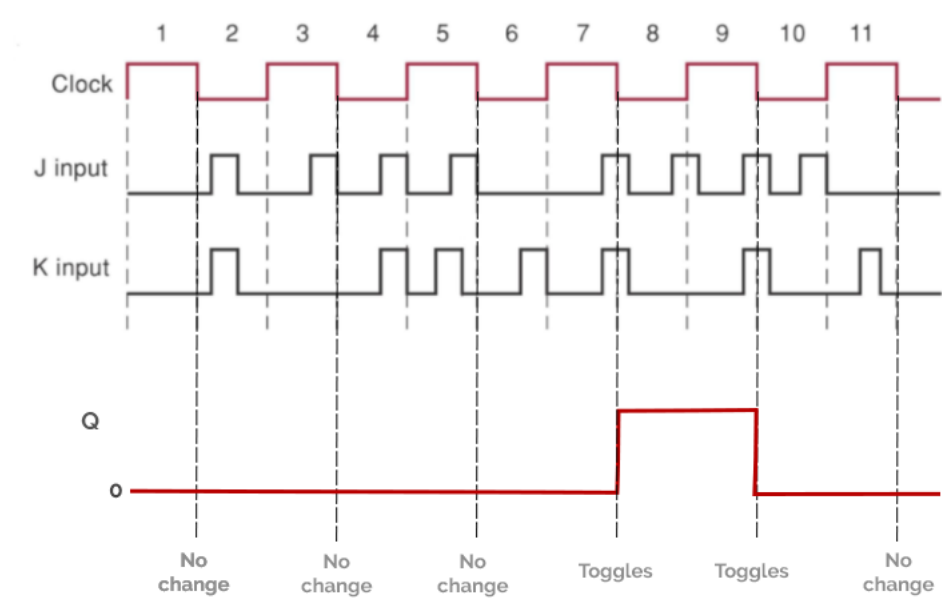

J	K	CLK	Q
0	0	↓	$Q_0$ (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	$\overline{Q_0}$ (toggles)

### Problem 3.7

Solution:

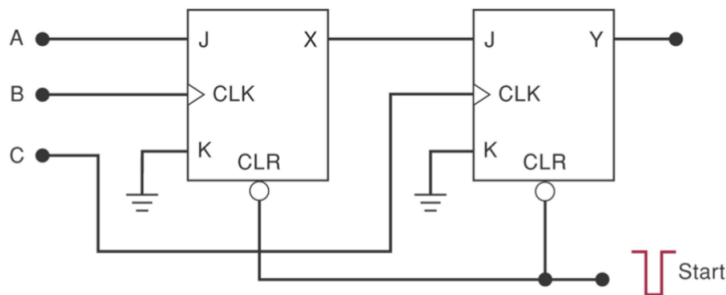

a)


The sequence that makes Y go HIGH is A, B, C because Y can go HIGH only when C goes HIGH while X is already HIGH. X can go HIGH only if B goes HIGH while A is HIGH.

b) Need for Start Pulse

We know that the outputs X and Y need to be cleared to 0 before applying the A, B and C signals. To clear the outputs, we need a negative going Start pulse at the R input. R of JK flip-flop is active LOW.

c)

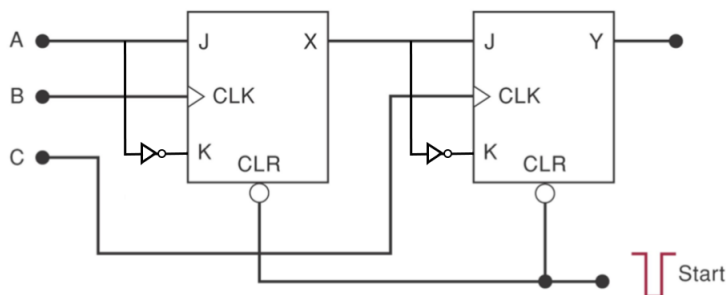A D Flip-Flop may be implemented with a J-K Flip-Flop by tying the J input to the K input through an inverter, as it is shown below:



which is equivalent to:

