

Homework 2

Problem 2.1

Solution:

a) $777_8 + 1_8 = 1000_8$

b) $888_{16} + 1_{16} = 889_{16}$

c) $32007_8 + 1_8 = 32010_8$

d) $32108_{16} + 1_{16} = 32109_{16}$


e) $8BFF_{16} + 1_{16} = 8C00_{16}$

f) $1219_{16} + 1_{16} = 121A_{16}$


Problem 2.2

Solution:


a) $X = \overline{A * B * (C + D)}$

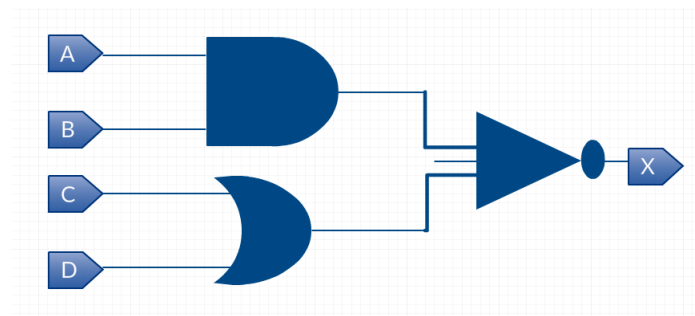

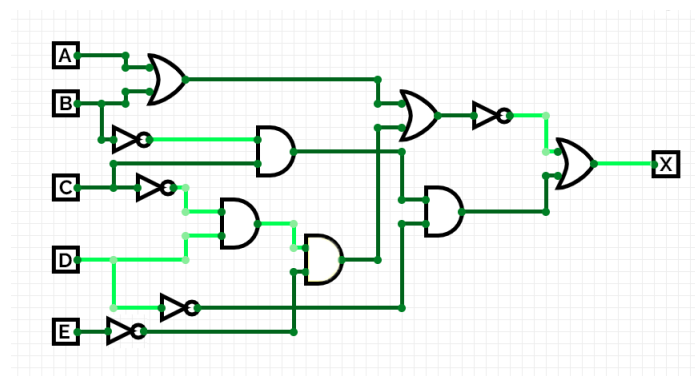
b) $X = \overline{A + B + \overline{C} * D * \overline{E}} + \overline{B} + C + \overline{D}$



c)

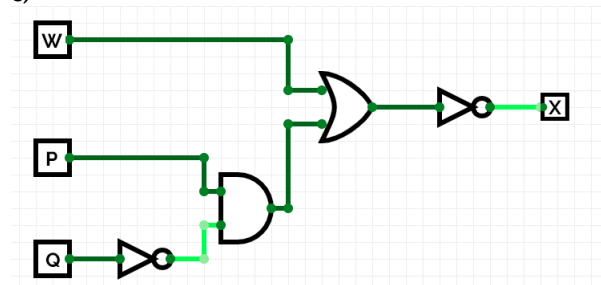

d)

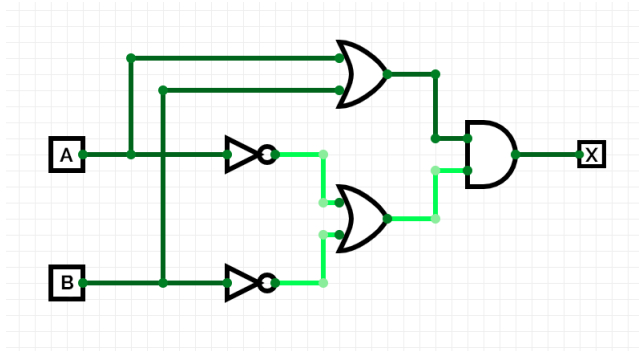

Problem 2.3

Solution:

$$R1 = \overline{M * N * Q}$$

$$R2 = \overline{M * \overline{N} * Q}$$

$$R3 = \overline{M * N * Q}$$

The truth table of the circuit:

M	N	Q	R1	R2	R3	X
0	0	0	1	1	1	0
0	0	1	1	1	1	0
0	1	0	1	1	1	0
0	1	1	1	1	0	1
1	0	0	1	1	1	0
1	0	1	1	0	1	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1

The sum of products: $X = \overline{M} * N * Q + M * \overline{N} * Q + M * N * Q$

Simplify:

$$X = \overline{M} * N * Q + M * \overline{N} * Q + M * N * Q =$$

$$\text{Distributive Law} := Q(\overline{M} * N + M * \overline{N} + M * N) =$$


$$\text{Distributive Law} := Q(\overline{M} * N + M * \overline{N} + M * N + M * N) =$$

$$\text{Distributive Law} := Q(N(\overline{M} + M) + M(\overline{N} + N)) =$$

$$\text{Identity Law} := Q(N * 1 + M * 1) =$$

$$\text{Distributive Law} := Q(N + M) = Q * N + Q * M$$

Circuit Representation after simplification:

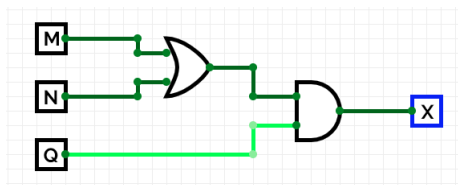

Problem 2.4

Solution:

a)

$$X + \overline{X} * Y = X + Y$$

$$X + \overline{X} * Y:$$

X	Y	\overline{X}	$\overline{X} \wedge Y$	$X \vee (\overline{X} \wedge Y)$
0	0	1	0	0
0	1	1	1	1
1	0	0	0	1
1	1	0	0	1

$$X + Y:$$

X	Y	$X \vee Y$
0	0	0
0	1	1
1	0	1
1	1	1

As it is evident, both sides of the equation result in the same output.

b)

$$\overline{X} + X * Y = \overline{X} + Y$$

$$\overline{X} + X * Y:$$

X	Y	\overline{X}	$X \wedge Y$	$\overline{X} \vee (X \wedge Y)$
0	0	1	0	1
0	1	1	0	1
1	0	0	0	0
1	1	0	1	1

$$\overline{X} + Y:$$

X	Y	\overline{X}	$\overline{X} \vee Y$
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

As it is evident, both sides of the equation result in the same output.

Problem 2.5

Solution:

a) $A + 1 = 1$

b) $A * A = A$

c) $B * \overline{B} = 0$

d) $C + C = C$

e) $X * 0 = 0$

f) $D * 1 = D$

g) $D + 0 = D$

h) $C + \overline{C} = 1$

i) $G + G * F = G$

j) $Y + \overline{W} * Y = Y$

Problem 2.6

Solution:

1. $\overline{W + Y} = \overline{W} * \overline{Y}$

W	Y	\overline{W}	\overline{Y}	$W + Y$	$\overline{W + Y}$	$\overline{W} * \overline{Y}$
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

2. $\overline{W * Y} = \overline{W} + \overline{Y}$

W	Y	\overline{W}	\overline{Y}	$W * Y$	$\overline{W * Y}$	$\overline{W} + \overline{Y}$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0

3. $1 + W = 1$

1	W	$1 \vee W$
1	0	1
1	0	1
1	1	1
1	1	1

4. $0 + W = W$

0	W	$1 \vee W$
0	0	0
0	0	0
0	1	1
0	1	1

5. $0 * W = 0$

0	W	$0 \wedge W$
0	0	0
0	0	0
0	1	0
0	1	0

6. $1 * W = W$

1	W	$1 \wedge W$
1	0	0
1	0	0
1	1	1
1	1	1

Problem 2.7

DL = Distributive Law
CL = Complement Law
IL = Identity Law

The sum-of-product expression:

$$X = \overline{A} * \overline{B} * \overline{C} * D + \overline{A} * \overline{B} * C * D + \overline{A} * B * \overline{C} * D + \overline{A} * B * C * D + A * \overline{B} * \overline{C} * \overline{D} + A * B * \overline{C} * \overline{D} + A * B * C * \overline{D} =$$

$$DL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * \overline{B} * \overline{C} + \overline{A} * \overline{B} * C + \overline{A} * B * \overline{C} + \overline{A} * B * C + A * \overline{B} * \overline{C} + A * B * \overline{C} + A * B * C) =$$

$$DL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * \overline{B} * (\overline{C} * C) + \overline{A} * B * (\overline{C} + C) + A * B * (\overline{C} + C)) =$$

$$CL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * \overline{B} * 1 + \overline{A} * B * 1 + A * B * 1) =$$

$$IL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * \overline{B} + \overline{A} * B + A * B)$$

Since $A + A = A$, write $\overline{A} * B = \overline{A} * B + \overline{A} * B$:

$$X = A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * \overline{B} + \overline{A} * B + \overline{A} * B + A * B) =$$

$$DL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * (\overline{B} + B) + B * (\overline{A} + A)) =$$

$$CL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} * 1 + B * 1) =$$

$$IL := A * \overline{B} * \overline{C} * \overline{D} + D(\overline{A} + B) =$$

$$DL := A * \overline{B} * \overline{C} * \overline{D} + \overline{A} * D + B * D$$

Problem 2.8

Solution:

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0	1	1	0
$\overline{A}B$	0	1 \wedge 1	1 \wedge 1	0
$A\overline{B}$	0	1	1	0
AB	1	0	0	0

Note: the 1s in the second row belong to both groups (red 1s and blue 1s) in order to give the minimalistic expression.

After building the Karnaugh-map using gray coding (00, 01, 11, 10) from the truth table given in **Problem 2.7**, we first try to create groups of 1s. We have 3 groups in total, distinguished by their colors (red, blue and green).

Green group (single 1): all terms are included $\Rightarrow A * \overline{B} * \overline{C} * \overline{D}$.

Blue group: $\overline{A} * D \Rightarrow$ These terms do not change regardless of the output.

Red group: similarly $\Rightarrow B * D$

As a result, we obtain: $X = A * \overline{B} * \overline{C} * \overline{D} + \overline{A} * D + B * D$